

Wind Explorer Li-Cor Pyranometer Connection

Introduction

The diagram below describes connection of the pyranometer and 150 ohm resistor to the Wind Explorer's terminal strip.

